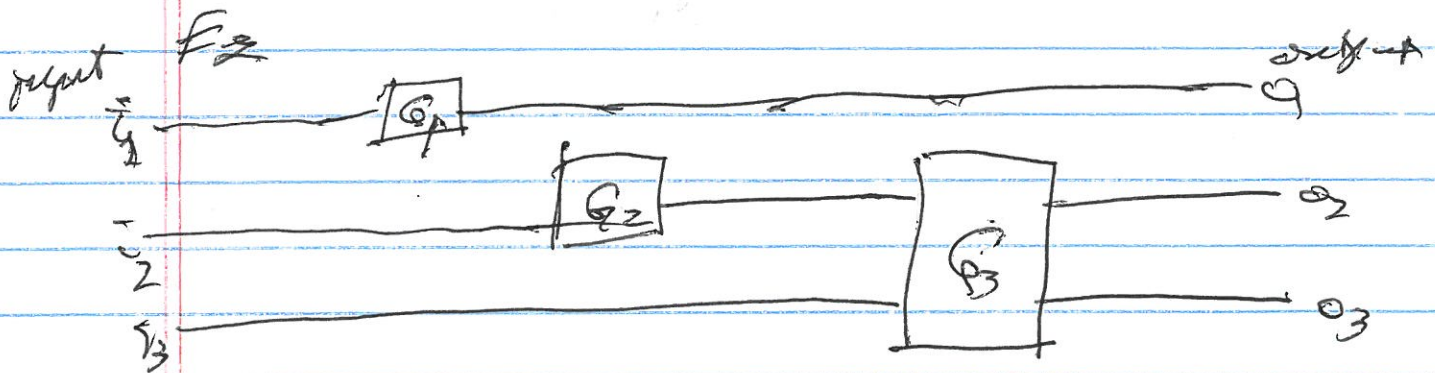


prob: least time we could find them; (how to find it?)
 & answer could be yes

Circuit model of ^(classical) computation

circuit: an array (or network) of gates

restricted to cyclic ^(no), reversible circuits



each line is a 'wire', each box represent a logic gate
 time t proceeds from left to right

circuit complexity may be measured by the # of gates, width ('space') — that is the # of wires, and depth, being the # of time-slices.
 (above depth 3, # of gates 3, and width 3)

for deterministic circuits, each bit is just 0 or 1. ^{in state}

for a probabilistic circuit can assign probs. p_0 to be in state 0, p_1 to be in state 1.

So a single bit may be associated w/ a 2-d vector
 $\begin{pmatrix} p_0 \\ p_1 \end{pmatrix}$

operations (gates) ^{on} state vectors may be written as matrices.

Eg logical NOT gate

we describe the action on basis states

$$\text{NOT} \begin{pmatrix} 1 \\ 0 \end{pmatrix} = \begin{pmatrix} 0 \\ 1 \end{pmatrix}, \quad \text{NOT} \begin{pmatrix} 0 \\ 1 \end{pmatrix} = \begin{pmatrix} 1 \\ 0 \end{pmatrix}$$

Thus the matrix repr of the NOT gate operator is

$$\text{NOT} = \begin{pmatrix} 0 & 1 \\ 1 & 0 \end{pmatrix}$$

For more general inputs (system) _{in some type!}

$$\text{NOT} \begin{pmatrix} p_0 \\ p_1 \end{pmatrix} = \begin{pmatrix} 0 & 1 \\ 1 & 0 \end{pmatrix} \begin{pmatrix} p_0 \\ p_1 \end{pmatrix} = \begin{pmatrix} p_1 \\ p_0 \end{pmatrix}$$

Suppose next two wires

$$\text{---} \begin{pmatrix} p_0 \\ p_1 \end{pmatrix}$$

$$\text{---} \begin{pmatrix} q_0 \\ q_1 \end{pmatrix} \quad \text{+ prob for each wire}$$

a set of basis states is

0	0
0	1
1	0
1	1

The combined state of the 2 qubits may be taken as

$$\begin{bmatrix} p_0 & q_0 \\ p_1 & q_1 \\ p_2 & q_2 \\ p_3 & q_3 \end{bmatrix} = \begin{pmatrix} p_0 \\ p_1 \\ p_2 \\ p_3 \end{pmatrix} \otimes \begin{pmatrix} q_0 \\ q_1 \\ q_2 \\ q_3 \end{pmatrix}$$

a first example of a tensor product of vectors. (much more on these products to come)

Other examples:

$$\begin{pmatrix} a & b \\ c & d \end{pmatrix} \otimes \begin{pmatrix} q \\ p \end{pmatrix}$$

$$= \begin{bmatrix} aq & bq \\ ap & bp \\ cq & dq \\ cp & dp \end{bmatrix}$$

$$\text{if } A = \begin{pmatrix} a & b \\ c & d \end{pmatrix}, \quad B = \begin{pmatrix} r & s \\ t & u \end{pmatrix}$$

$$A \otimes B = \begin{pmatrix} a \begin{pmatrix} r & s \\ t & u \end{pmatrix} & b \begin{pmatrix} r & s \\ t & u \end{pmatrix} \\ c \begin{pmatrix} r & s \\ t & u \end{pmatrix} & d \begin{pmatrix} r & s \\ t & u \end{pmatrix} \end{pmatrix}$$

amounts to $(A_1 \otimes A_2)(B_1 \otimes B_2) = A_1 B_1 \otimes A_2 B_2$

Back to a 2-qubit circuit

Consider action of controlled-NOT (or CNOT) gate.


Has 2 inputs - the control & target bits
The target bit is flipped only if the control bit is in the state 1

← need 2 additions, as the XOR gate

C	t	output C	output C ⊕ t
0	0	0	0
0	1	0	1
1	0	1	1
1	1	1	0

(points in the 2 states)
(5 unique values for 2 states)

matrix repr. (2x2)

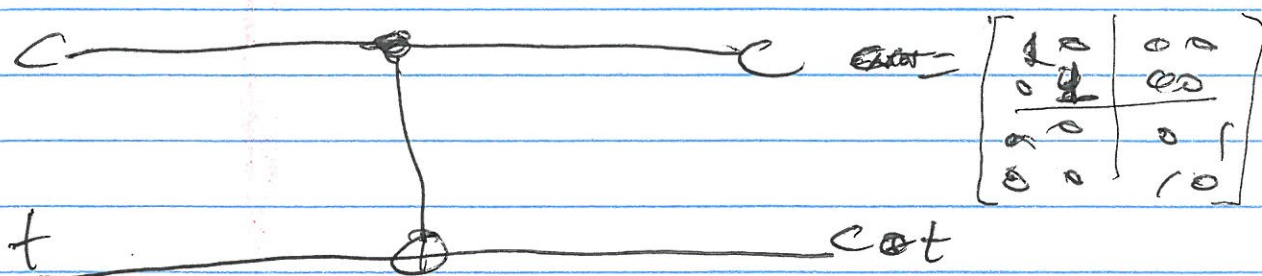

so if first bit is in state $\begin{pmatrix} 1 \\ 0 \end{pmatrix}$ & the 2nd bit in state

$$\begin{pmatrix} 1 \\ 0 \end{pmatrix}, \text{ then } \begin{pmatrix} 1 \\ 0 \end{pmatrix} \otimes \begin{pmatrix} 1 \\ 0 \end{pmatrix} = \begin{pmatrix} 1 \\ 0 \\ 0 \\ 0 \end{pmatrix}$$

$$\& \text{CNOT} \begin{pmatrix} 1 \\ 0 \\ 0 \\ 0 \end{pmatrix} = \frac{1}{2} \begin{pmatrix} 1 \\ 0 \\ 0 \\ 1 \end{pmatrix}$$

which is not a tensor product state -
Correlation bits in classical case
-entangled in quantum setting

CNOT Summary

$$CNOT : (a, b) \rightarrow (a, a \oplus b)$$

note if the target bit is 0, CNOT leaves it alone:
 $(a, 0) \rightarrow (a, a)$

what's its inverse - for class to consider
 (can use matrix representation eg. 2 unitary matrices)

$$L \begin{pmatrix} a & b \\ c & d \end{pmatrix} = \frac{1}{ad-bc} \begin{pmatrix} d & -b \\ -c & a \end{pmatrix}$$

$$U_{CNOT} = \begin{pmatrix} I_2 & 0 \\ 0 & NOT \end{pmatrix} \Rightarrow U_{CNOT}^{-1} = I_2$$

is the ~~inverse~~ 2 operators of CNOT:


$$(a, b) \rightarrow (a, a \oplus b) \rightarrow (a, a \oplus (a \oplus b)) = (a, b)$$

a	b	a' = a	b' = a ⊕ b	a ⊕ (a ⊕ b)
0	0	0	0	0
0	1	0	1	1
1	0	1	1	0
1	1	1	0	1

Pr. $(CNOT)^{-1} = CNOT$
 (CNOT is its own inverse)


the CNOT gate is self inverse

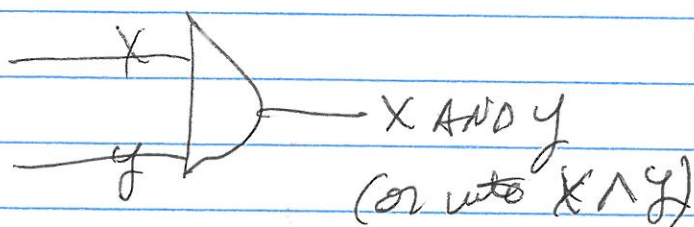Reversible computation - examples) start from NOT & CNOT




is reversible in this form

reversible version:

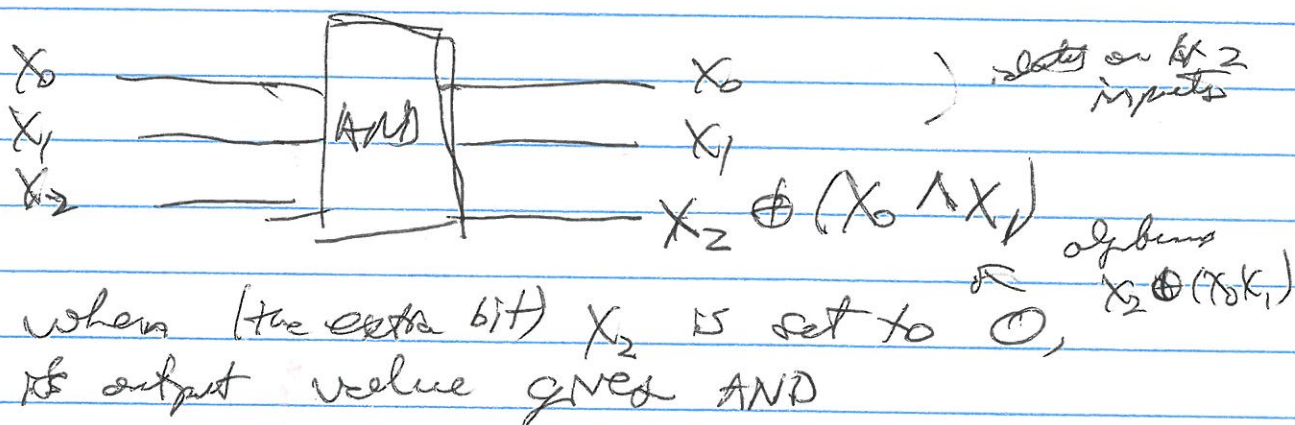

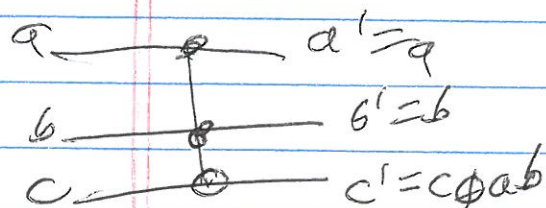This is an instance of the 3-input, 3-output Toffoli gate (C^2 -NOT gate)



If we put $a=1$, we get CNOT

(C^2 -NOT or Toffoli gate is also self reverse)

a	b	c	a'	b'	c'
0	0	0	0	0	0
0	0	1	0	0	1
0	1	0	0	1	0
0	1	1	0	1	1
1	0	0	1	0	0
1	0	1	1	0	1
1	1	0	1	1	1
1	1	1	1	1	0

Identify and the 6 gates

Supplement to in-class example

* we had $a \text{ NAND } a \equiv \text{NOT}(a \text{ AND } a)$
 $\equiv 1 - a^2 \equiv 1 - a \equiv \text{NOT}(a)$

now w/ truth table(s):

a	$a \text{ AND } a$	$\text{NOT}(a \text{ AND } a)$	$\text{NOT}(a)$
0	0	1	1
1	1	0	0

these two columns agree

* ↗

Good morning but le monde (everyone)

we had a long weekend, so perhaps
 we should review a bit first

a point concerning the circuit model
 - using just 4 wires for now;



note the order of matrix operations as the input
 state:


$$G_3 G_2 \text{ NOT } G_1 \begin{pmatrix} p_0 \\ p_1 \end{pmatrix}$$

A reversible method for computing f

(In principle) can always find a reversible circuit for a computation (ie. for a NWay CN circuit)

reversible

Fig 1.6 plot

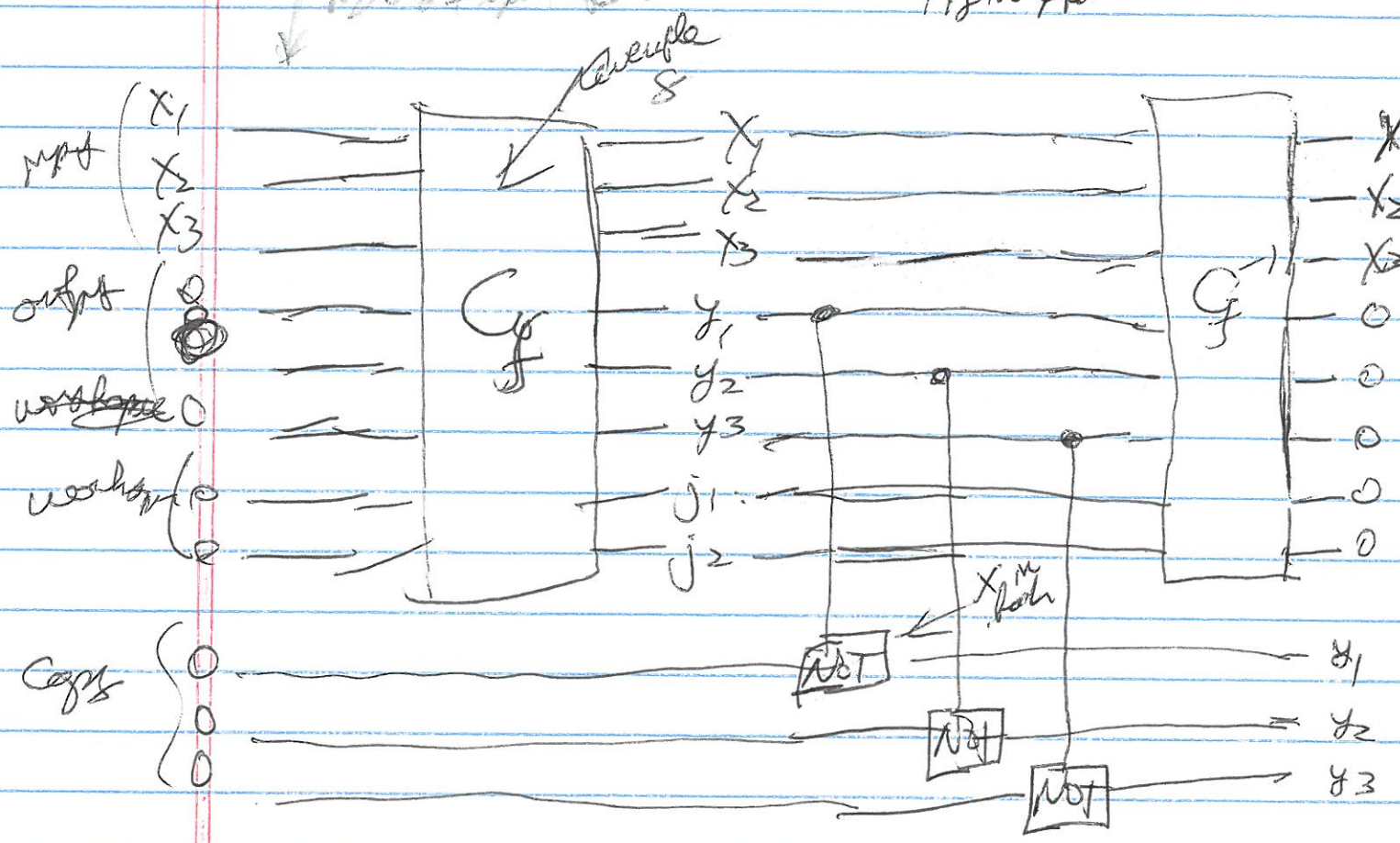

where $f(x_1, x_2, x_3) = (y_1, y_2, y_3)$

recall NOT gate if 0 as the target bit:

But do:

c	t	$c \oplus t$
0	0	0
1	0	1

$\leftarrow c \oplus t$ then copies the value of the control gate

Ex. 15.13 pp 14-15 handover principle here a window David worked!

Any reversible fn $f: \{0,1\}^m \rightarrow \{0,1\}^n$
 can be embedded into a reversible fn.

Define the fn $\tilde{f}: \{0,1\}^{m+n} \rightarrow \{0,1\}^{m+n}$

such that $\tilde{f}(x, y) = (x, [y + f(x)] \pmod{2^n})$

where x represents m bits, while y and $f(x)$ repr n bits.
 Since \tilde{f} takes distinct inputs into distinct outputs,
 it is an invertible $(m+n)$ -bit function


^(17.61) Landauer's principle. Each time a single bit of info ^(lower bound)
 is erased, the amount of energy dissipated
 into the environment is at least $k_B T \ln 2$,
 where $k_B \approx 1.38 \times 10^{-23} \text{ J/K} = 1.38 \times 10^{-23} \text{ J/K}$ ($1 \text{ J} = 10^7 \text{ erg}$)
 and T the (absolute) temp. of the (surrounding)
 environment. Equivalently, we say that the entropy
 of the environment increases by at least $k_B \ln 2$.

Extracting work from information:

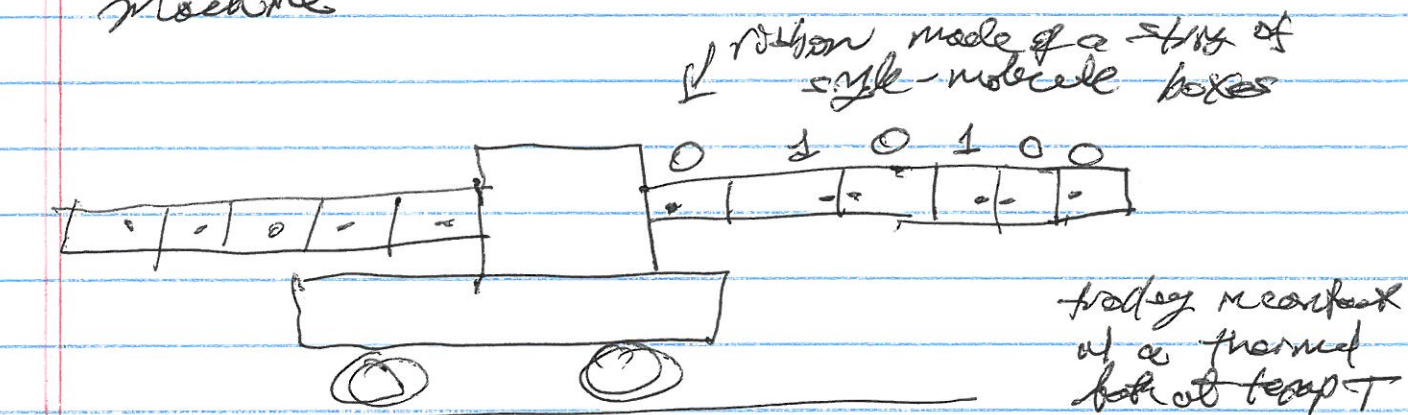
C. Bennett's example

9

showing that info may be used as fuel to move a machine



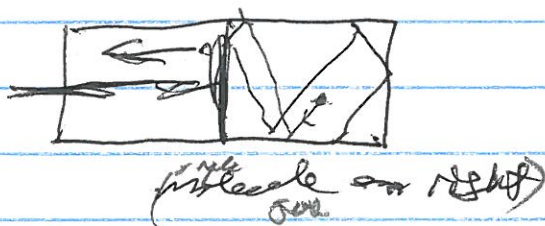we can extract work to move the trolley by
inserting a piston in the middle of each box



extracted work is $W = k_B T \ln 2$

For a N -bit ribbon, the total work is

$N k_B T \ln 2$ (and it may be used to displace the trolley). When the ribbon comes out of the trolley, the molecules can be anywhere inside the volume V .